

# Relatório

Tópico: Aulas 4 & 5 - Contadores

Grupo: Adhemar Molon Neto

14687681

Alessandro Rodrigues Pereira da Silva

15436838

Link do Github: <>

## Parte 1

### Descrição

Foi desenvolvido em VHDL um contador de 8 bits, usando oito instâncias de flip-flops tipo T, de modos que cada um muda seu valor quando a anterior muda 2 vezes. Foram usados aproximadamente 102 elementos lógicos e 33 pins.

### Códigos VHDL

#### d\_latch.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity d_latch is
    port(
        Data, Clock      : in std_logic;
        Qu, notQu        : out std_logic
    );
END d_latch;
ARCHITECTURE main of d_latch is
    signal R_g, S_g, Qa, Qb : std_logic;
    attribute keep : boolean;
    attribute keep of R_g, S_g, Qa, Qb : signal is true;
begin
    S_g <= not (Data and Clock);
    R_g <= not ((not Data) and Clock);
    Qa <= not (S_g and Qb);
    Qb <= not (R_g and Qa);
    Qu <= Qa;
    notQu <= Qb;
END main;
```

#### d\_flip\_flop.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

ENTITY d_flip_flop is
    port(
        D, Clk      : in std_logic;
        Q, nQ       : out std_logic
    );
```

```

    );
END d_flip_flop;
ARCHITECTURE Behavioral of d_flip_flop is
    COMPONENT d_latch is
        port(
            Data, Clock      : in std_logic;
            Qu, notQu       : out std_logic
        );
    END COMPONENT;
    signal Qm, Qs : std_logic;
    signal nClk : std_logic;
    attribute keep : boolean;
    attribute keep of Qm, Qs : signal is true;
begin
    nClk <= not Clk;
    Master: entity work.d_latch
        port map (
            Data => D,
            Clock => nClk,
            Qu => Qm,
            notQu => open
        );
    Slave: entity work.d_latch
        port map (
            Data => Qm,
            Clock => Clk,
            Qu => Qs,
            notQu => open
        );
    Q <= Qs;
    nQ <= not Qs;
END Behavioral;

```

### **t\_flip\_flop\_clear.vhd**

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
ENTITY t_flip_flop_clear IS
    port(
        T, Clock, Clr      : in std_logic;
        Qu, notQu         : out std_logic
    );
END t_flip_flop_clear;
ARCHITECTURE Behavioral OF t_flip_flop_clear IS
    signal Data : std_logic;
    signal Qf: std_logic;
    component d_flip_flop is
        port(
            D, Clk      : in std_logic;
            Q, nQ       : out std_logic

```

```

        );
    end component;
begin
    Data <= (not Clr) and (T xor Qf);
    d1 : entity work.d_flip_flop
        port map(
            D => Data,
            Clk => Clock,
            Q => Qf,
            nQ => notQu
        );
    Qu <= Qf;

END Behavioral;

ex1.vhd
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

ENTITY ex1 is
    port(
        Enable, Clk, Clear          : in std_logic;
        b0,b1,b2,b3,b4,b5,b6,b7    : out std_logic;
        num                          : out
std_logic_vector(7 downto 0);
        hex0                        : out
std_logic_vector(6 downto 0);
        hex1                        : out
std_logic_vector(6 downto 0)
    );
END ex1;

ARCHITECTURE main of ex1 is
    COMPONENT t_flip_flop_clear IS
        port(
            T, Clock, Clr           : in std_logic;
            Qu, notQu               : out std_logic
        );
    END COMPONENT;
    COMPONENT hex_display IS
        port(
            num4 : in std_logic_vector(3 downto 0);
            hex  : out std_logic_vector(6 downto 0)
        );
    END COMPONENT;

    signal E1, E2, E3, E4, E5, E6, E7 : std_logic;
    signal Q0, Q1, Q2, Q3, Q4, Q5, Q6, Q7 : std_logic;
    signal nClear : std_logic;
    signal num8 : std_logic_vector(7 downto 0);
begin

```

```

nClear <= not Clear;
E1 <= Enable and Q0;
E2 <= E1 and Q1;
E3 <= E2 and Q2;
E4 <= E3 and Q3;
E5 <= E4 and Q4;
E6 <= E5 and Q5;
E7 <= E6 and Q6;
tff1 : entity work.t_flip_flop_clear
    port map(
        T => Enable,
        Clock => Clk,
        Clr => nClear,
        Qu => Q0,
        notQu => open
    );
tff2 : entity work.t_flip_flop_clear
    port map(
        T => E1,
        Clock => Clk,
        Clr => nClear,
        Qu => Q1,
        notQu => open
    );
tff3 : entity work.t_flip_flop_clear
    port map(
        T => E2,
        Clock => Clk,
        Clr => nClear,
        Qu => Q2,
        notQu => open
    );
tff4 : entity work.t_flip_flop_clear
    port map(
        T => E3,
        Clock => Clk,
        Clr => nClear,
        Qu => Q3,
        notQu => open
    );
tff5 : entity work.t_flip_flop_clear
    port map(
        T => E4,
        Clock => Clk,
        Clr => nClear,
        Qu => Q4,
        notQu => open
    );

```

```

tff6 : entity work.t_flip_flop_clear
    port map(
        T => E5,
        Clock => Clk,
        Clr => nClear,
        Qu => Q5,
        notQu => open
    );
tff7 : entity work.t_flip_flop_clear
    port map(
        T => E6,
        Clock => Clk,
        Clr => nClear,
        Qu => Q6,
        notQu => open
    );
tff8 : entity work.t_flip_flop_clear
    port map(
        T => E7,
        Clock => Clk,
        Clr => nClear,
        Qu => Q7,
        notQu => open
    );

b0 <= Q0;
b1 <= Q1;
b2 <= Q2;
b3 <= Q3;
b4 <= Q4;
b5 <= Q5;
b6 <= Q6;
b7 <= Q7;
num8(0) <= Q0;
num8(1) <= Q1;
num8(2) <= Q2;
num8(3) <= Q3;
num8(4) <= Q4;
num8(5) <= Q5;
num8(6) <= Q6;
num8(7) <= Q7;
num <= num8;
hd0 : entity work.hex_display
    port map(
        num4 => num8(3 downto 0),
        hex => hex0
    );
hd1 : entity work.hex_display

```

```

        port map(
            num4 => num8(7 downto 4),
            hex => hex1
        );


end main;

hex_display.vhd
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;


ENTITY hex_display IS
    port(
        num4 : in std_logic_vector(3 downto 0);
        hex   : out std_logic_vector(6 downto 0)
    );
END hex_display;
ARCHITECTURE Behavioral OF hex_display IS
begin
    with num4 select
        hex <=
            "1000000" when "0000", -- 0
            "1111001" when "0001", -- 1
            "0100100" when "0010", -- 2
            "0110000" when "0011", -- 3
            "0011001" when "0100", -- 4
            "0010010" when "0101", -- 5
            "0000010" when "0110", -- 6
            "1111000" when "0111", -- 7
            "0000000" when "1000", -- 8
            "0010000" when "1001", -- 9
            "0001000" when "1010", -- A
            "0000011" when "1011", -- B
            "1000110" when "1100", -- C
            "0100001" when "1101", -- D
            "0000110" when "1110", -- E
            "0001110" when "1111", -- F
            "1111111" when others;
END Behavioral;

```

## Simulação no ModelSim

 

## RTL Viewer

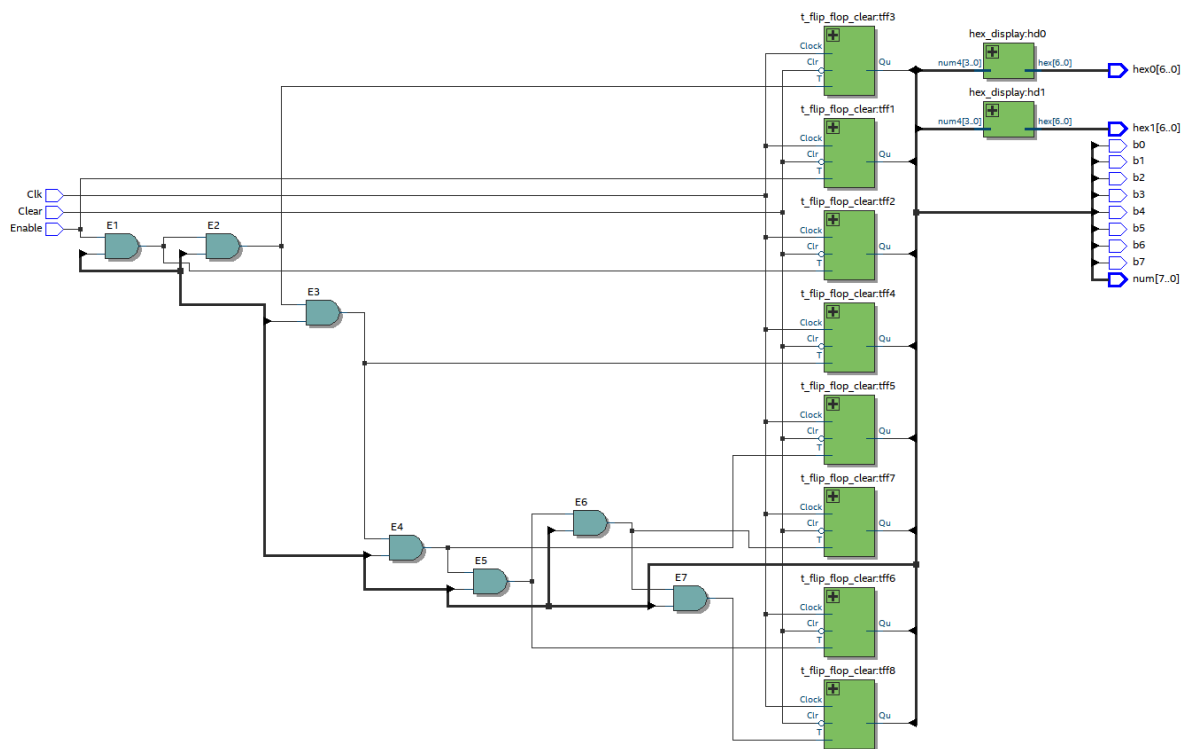

## Parte 2

### Descrição

Foi desenvolvido um contador de 16 bits em VHDL utilizando flip-flops tipo T. Cada flip-flop foi configurado para mudar seu estado com base no sinal do anterior. Este design empregou aproximadamente 204 elementos lógicos e 47 pinos.

### Código VHDL (com flip-flops)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

ENTITY aulas4e5part2 is
    port(
        Enable, Clk, Clear          : in std_logic;
        num                          : out
        std_logic_vector(15 downto 0);
        hex0                        : out
        std_logic_vector(6 downto 0);
        hex1                        : out
        std_logic_vector(6 downto 0);
        hex2                        : out
        std_logic_vector(6 downto 0);
        hex3                        : out
        std_logic_vector(6 downto 0)
    );
END aulas4e5part2;
ARCHITECTURE main of aulas4e5part2 is
```

```

COMPONENT t_flip_flop_clear IS
    port(
        T, Clock, Clr          : in std_logic;
        Qu, notQu              : out std_logic
    );
END COMPONENT;

COMPONENT hex_display IS
    port(
        num4 : in std_logic_vector(3 downto 0);
        hex   : out std_logic_vector(6 downto 0)
    );
END COMPONENT;

signal E : std_logic_vector(15 downto 0);
signal Q : std_logic_vector(15 downto 0);
signal nClear : std_logic;
signal num8 : std_logic_vector(15 downto 0);
begin
    nClear <= not Clear;
    E(1) <= Enable and Q(0);
    E(2) <= E(1) and Q(1);
    E(3) <= E(2) and Q(2);
    E(4) <= E(3) and Q(3);
    E(5) <= E(4) and Q(4);
    E(6) <= E(5) and Q(5);
    E(7) <= E(6) and Q(6);
    E(8) <= E(7) and Q(7);
    E(9) <= E(8) and Q(8);
    E(10) <= E(9) and Q(9);
    E(11) <= E(10) and Q(10);
    E(12) <= E(11) and Q(11);
    E(13) <= E(12) and Q(12);
    E(14) <= E(13) and Q(13);
    E(15) <= E(14) and Q(14);
    tff1 : entity work.t_flip_flop_clear
        port map(
            T => Enable,
            Clock => Clk,
            Clr => nClear,
            Qu => Q(0),
            notQu => open
        );
    tff2 : entity work.t_flip_flop_clear
        port map(
            T => E(1),
            Clock => Clk,
            Clr => nClear,
            Qu => Q(1),
            notQu => open
        );

```



```

    );
tff3 : entity work.t_flip_flop_clear
port map(
    T => E(2),
    Clock => Clk,
    Clr => nClear,
    Qu => Q(2),
    notQu => open
);
tff4 : entity work.t_flip_flop_clear
port map(
    T => E(3),
    Clock => Clk,
    Clr => nClear,
    Qu => Q(3),
    notQu => open
);
tff5 : entity work.t_flip_flop_clear
port map(
    T => E(4),
    Clock => Clk,
    Clr => nClear,
    Qu => Q(4),
    notQu => open
);
tff6 : entity work.t_flip_flop_clear
port map(
    T => E(5),
    Clock => Clk,
    Clr => nClear,
    Qu => Q(5),
    notQu => open
);
tff7 : entity work.t_flip_flop_clear
port map(
    T => E(6),
    Clock => Clk,
    Clr => nClear,
    Qu => Q(6),
    notQu => open
);
tff8 : entity work.t_flip_flop_clear
port map(
    T => E(7),
    Clock => Clk,
    Clr => nClear,
    Qu => Q(7),
    notQu => open

```

```

);
tff9 : entity work.t_flip_flop_clear
port map(
    T => E(8),
    Clock => Clk,
    Clr => nClear,
    Qu => Q(8),
    notQu => open
);
tff10 : entity work.t_flip_flop_clear
port map(
    T => E(9),
    Clock => Clk,
    Clr => nClear,
    Qu => Q(9),
    notQu => open
);
tff11 : entity work.t_flip_flop_clear
port map(
    T => E(10),
    Clock => Clk,
    Clr => nClear,
    Qu => Q(10),
    notQu => open
);
tff12 : entity work.t_flip_flop_clear
port map(
    T => E(11),
    Clock => Clk,
    Clr => nClear,
    Qu => Q(11),
    notQu => open
);
tff13 : entity work.t_flip_flop_clear
port map(
    T => E(12),
    Clock => Clk,
    Clr => nClear,
    Qu => Q(12),
    notQu => open
);
tff14 : entity work.t_flip_flop_clear
port map(
    T => E(13),
    Clock => Clk,
    Clr => nClear,
    Qu => Q(13),
    notQu => open

```

```

    );
tff15 : entity work.t_flip_flop_clear
    port map(
        T => E(14),
        Clock => Clk,
        Clr => nClear,
        Qu => Q(14),
        notQu => open
    );
tff16 : entity work.t_flip_flop_clear
    port map(
        T => E(15),
        Clock => Clk,
        Clr => nClear,
        Qu => Q(15),
        notQu => open
    );

num8 <= Q;
num <= num8;
hd0 : entity work.hex_display
    port map(
        num4 => num8(3 downto 0),
        hex => hex0
    );
hd1 : entity work.hex_display
    port map(
        num4 => num8(7 downto 4),
        hex => hex1
    );
hd2 : entity work.hex_display
    port map(
        num4 => num8(11 downto 8),
        hex => hex2
    );
hd3 : entity work.hex_display
    port map(
        num4 => num8(15 downto 12),
        hex => hex3
    );

```

```

end main;

```

### **Código VHDL (usando aritmética)**

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

use IEEE.NUMERIC_STD.ALL;

```

```

ENTITY part2 is
    port(
        Enable, Clk, Clear    : in std_logic;
        hex0,hex1,hex2,hex3    : out std_logic_vector(6 downto 0)
    );
END part2;
ARCHITECTURE main of part2 is
    COMPONENT hex_display IS
        port(
            num4 : in std_logic_vector(3 downto 0);
            hex   : out std_logic_vector(6 downto 0)
        );
    END COMPONENT;
    signal Qvec : std_logic_vector(15 downto 0);
    signal num0,num1,num2,num3 : std_logic_vector(3 downto 0);
begin
    process (Clk) is
    begin
        if(rising_edge(Clk)) then
            if(Clear = '0') then
                Qvec <= "0000000000000000";
            elsif (Enable = '1') then
                if(unsigned(Qvec) < 65536) then
                    Qvec <= std_logic_vector(unsigned(Qvec) + 1);
                else
                    Qvec <= "0000000000000000";
                end if;
            end if;
        end if;
    end process;
    num0 <= Qvec(3 downto 0);
    num1 <= Qvec(7 downto 4);
    num2 <= Qvec(11 downto 8);
    num3 <= Qvec(15 downto 12);
    hd0 : entity work.hex_display
        port map(
            num4 => num0,
            hex => hex0
        );
    hd1 : entity work.hex_display
        port map(
            num4 => num1,
            hex => hex1
        );
    hd2 : entity work.hex_display
        port map(
            num4 => num2,

```

```


        hex => hex2
    );
    hd3 : entity work.hex_display
    port map(
        num4 => num3,
        hex => hex3
    );

end main;


```

## RTL Viewer

com flip-flops:

 

com aritmética:

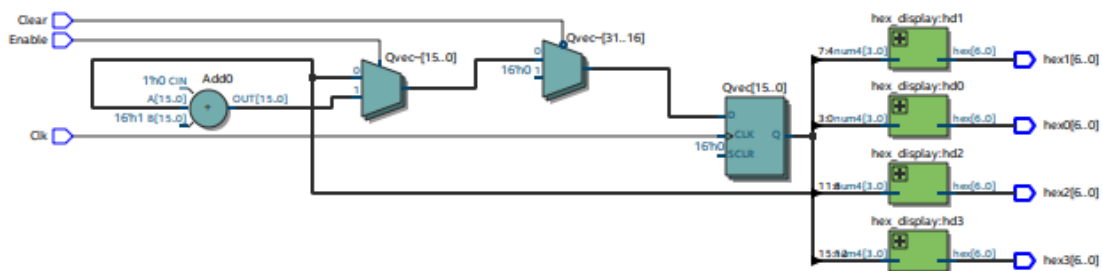

## Parte 3

### Descrição

Foi implementado em VHDL um contador decimal com variável de 26 bits, utilizado para gerenciar ciclos de contagem. A lógica assegura a reinicialização após alcançar 9. O código resultante emprega técnicas para controle de tempo, incluindo exibição em um único display hexadecimal.

### Código VHDL

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

use IEEE.NUMERIC_STD.ALL;

ENTITY part3comvar is
    port(
        Enable, Clk, Clear    : in std_logic;
        hex0                   : out std_logic_vector(6
downto 0)
    );
END part3comvar;
ARCHITECTURE main of part3comvar is
    COMPONENT hex_display IS
        port(
            num4 : in std_logic_vector(3 downto 0);
            hex   : out std_logic_vector(6 downto 0)
        );
    END COMPONENT;
    signal Qvec : std_logic_vector(25 downto 0);
    signal cont : std_logic_vector(3 downto 0);
    signal num  : std_logic_vector(3 downto 0);
begin
    process (Clk) is
    begin
        if(rising_edge(Clk)) then
            if(Clear = '0') then
                Qvec <= "00000000000000000000000000000000";
```

```


        cont <= "0000";
    elsif (Enable = '1') then
        if(unsigned(Qvec) < 500000000) then
            Qvec <= std_logic_vector(unsigned(Qvec) + 1);
        else
            Qvec <= "00000000000000000000000000000000";
            if(unsigned(cont) < 9) then
                cont <= std_logic_vector(unsigned(cont)
+ 1);

            else
                cont <= "0000";
            end if;
        end if;
    end if;
end if;
end process;
num <= cont;
hd0 : entity work.hex_display
    port map(
        num4 => num,
        hex => hex0
    );

end main;

```

## RTL Viewer

 

## Parte IV

### Descrição

Foi desenvolvido em VHDL um contador com lógica para exibição de uma sequência rotativa de palavras em displays hexadecimais. Utilizando um vetor de 26 bits para controle de tempo e um contador de 2 bits, o design permite a rotação cíclica de quatro estados. A implementação utiliza aproximadamente 4 displays hexadecimais para exibição sequencial.

## Código VHDL

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

use IEEE.NUMERIC_STD.ALL;

ENTITY part4 is
    port(
        Enable, Clk, Clear    : in std_logic;
        hex0,hex1,hex2,hex3    : out std_logic_vector(6 downto 0)
    );
END part4;
ARCHITECTURE main of part4 is
    signal Tempo : std_logic_vector(25 downto 0);
    signal cont : std_logic_vector(1 downto 0);

    type ARRAY_PALAVRA is array (0 to 3) of std_logic_vector(6 downto 0);
    constant word : ARRAY_PALAVRA := (0 => "1111111", 1 => "0100001",
    2 => "0000110", 3 => "1000000");

begin
    process (Clk) is
    begin
        if(rising_edge(Clk)) then
            if(Clear = '0') then
                Tempo <= "00000000000000000000000000000000";
                cont <= "00";
            elsif (Enable = '1') then
                if(unsigned(Tempo) < 50000000) then
                    Tempo <= std_logic_vector(unsigned(Tempo) +
1);

                    else
                        Tempo <= "00000000000000000000000000000000";
                        if(unsigned(cont) < 3) then
                            cont <= std_logic_vector(unsigned(cont)
+ 1);

                                else
                                    cont <= "00";
                                end if;
                            end if;
                        end if;
                    end if;
                end if;
            end process;
            hex3 <= word(to_integer(unsigned(cont)));
            hex2 <= word(to_integer(unsigned(cont) + 1) mod 4);
            hex1 <= word(to_integer(unsigned(cont) + 2) mod 4);
```



```

        hex0 <= word(to_integer(unsigned(cont) + 3) mod 4);

end main;

```

## Part V

### Descrição

Foi implementado um contador rotativo mais avançado em VHDL, utilizando lógica semelhante à parte 4, mas com 6 estados diferentes exibidos em 6 displays hexadecimais. O design inclui um vetor de 26 bits para controle de tempo e um contador de 3 bits, permitindo uma rotação contínua entre os estados definidos.

### Código VHDL

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

use IEEE.NUMERIC_STD.ALL;

ENTITY part5 is
    port(
        Enable, Clk, Clear          : in std_logic;
        hex0,hex1,hex2,hex3,hex4,hex5 : out std_logic_vector(6
downto 0)
    );
END part5;
ARCHITECTURE main of part5 is
    signal Tempo : std_logic_vector(25 downto 0);
    signal cont : std_logic_vector(2 downto 0);

    type ARRAY_PALAVRA is array (0 to 5) of std_logic_vector(6 downto
0);
    constant word : ARRAY_PALAVRA := (0 => "1111111", 1 => "1111111",
2 => "1111111", 3 => "0100001", 4 => "0000110", 5 => "1000000");

begin
    process (Clk) is
    begin
        if(rising_edge(Clk)) then
            if(Clear = '0') then
                Tempo <= "00000000000000000000000000000000";
                cont <= "000";
            end if;
        end if;
    end process;

```

```

        elsif (Enable = '1') then
            if(unsigned(Tempo) < 50000000) then
                Tempo <= std_logic_vector(unsigned(Tempo) +
1);

                else
                    Tempo <= "00000000000000000000000000000000";
                    if(unsigned(cont) < 5) then
                        cont <= std_logic_vector(unsigned(cont)
+ 1);

                        else
                            cont <= "000";
                        end if;
                    end if;
                end if;
            end if;
        end process;
        hex5 <= word(to_integer(unsigned(cont)));
        hex4 <= word(to_integer(unsigned(cont) + 1) mod 6);
        hex3 <= word(to_integer(unsigned(cont) + 2) mod 6);
        hex2 <= word(to_integer(unsigned(cont) + 3) mod 6);
        hex1 <= word(to_integer(unsigned(cont) + 4) mod 6);
        hex0 <= word(to_integer(unsigned(cont) + 5) mod 6);

end main;

```